

# **DIGITAL SYSTEM DESIGN USING VERILOG**

**COURSE CODE: 19EC5DCDSV  
(3 CREDITS)**

## **MODULE 3A**

1

**Faculty In-Charge: Dr. Dinesha P**



**[drdinesh-ece@dayanandasagar.edu](mailto:drdinesh-ece@dayanandasagar.edu)**

# SEQUENTIAL BASICS

- Sequential circuits
  - Outputs depend on current inputs and previous inputs
  - Store *state*: an abstraction of the history of inputs
- Usually governed by a periodic clock signal
  
# D-FLIP FLOPS



- 1-bit storage element
  - We will treat it as a basic component
  - The flip-flop is edge-triggered, meaning that on each rising edge of the clk input, the current value of the D input is stored within the flip-flop and reflected on the Q output




- Other kinds of flipflops
  - SR (set/reset), JK, T (toggle)
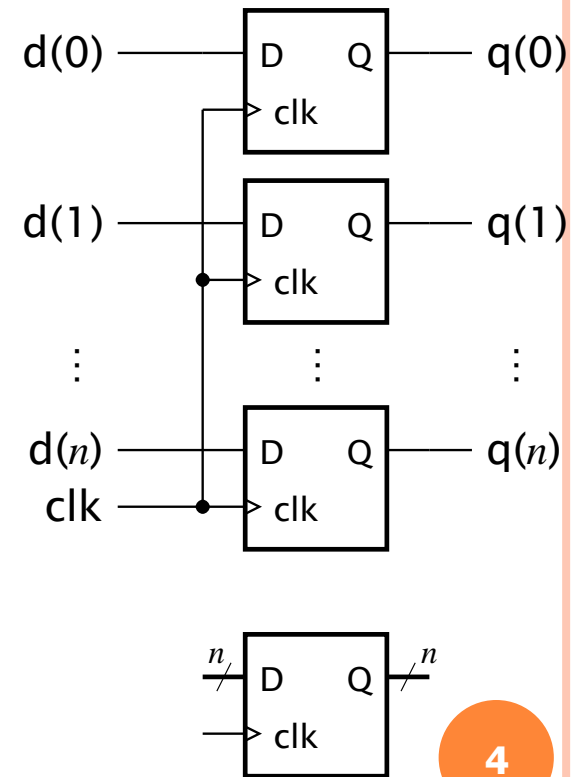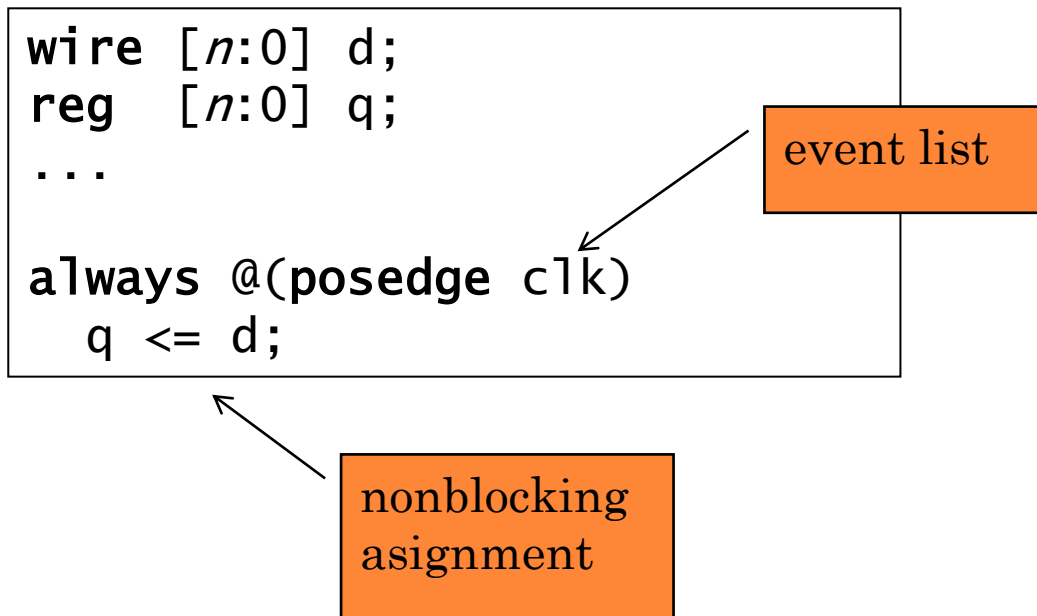
# REGISTERS:

- A group of flip-flops used in this way is called a *register*. *Each flip-flop in the register stores one bit of the code word of the stored value,*
- Store a multi-bit encoded value
  - One D-flipflop per bit
  - Stores a new value on each clock cycle


 
# A SIMPLE CIRCUIT USING BLOCKING ASSIGNMENT




```
module simple (x1, x2, x3,  
Clock, f, g);  
  input x1, x2, x3, Clock;  
  output reg f, g;  
  
  always @(posedge Clock)  
  begin  
    f = x1 & x2;  
    g = f | x3;  
  end
```

A rising edge, latch  $f = x_1 \& x_2$ , and  
latch  $g = (x_1 \& x_2) \mid x_3$ .

```
endmodule
```



# NON-BLOCKING ASSIGNMENT

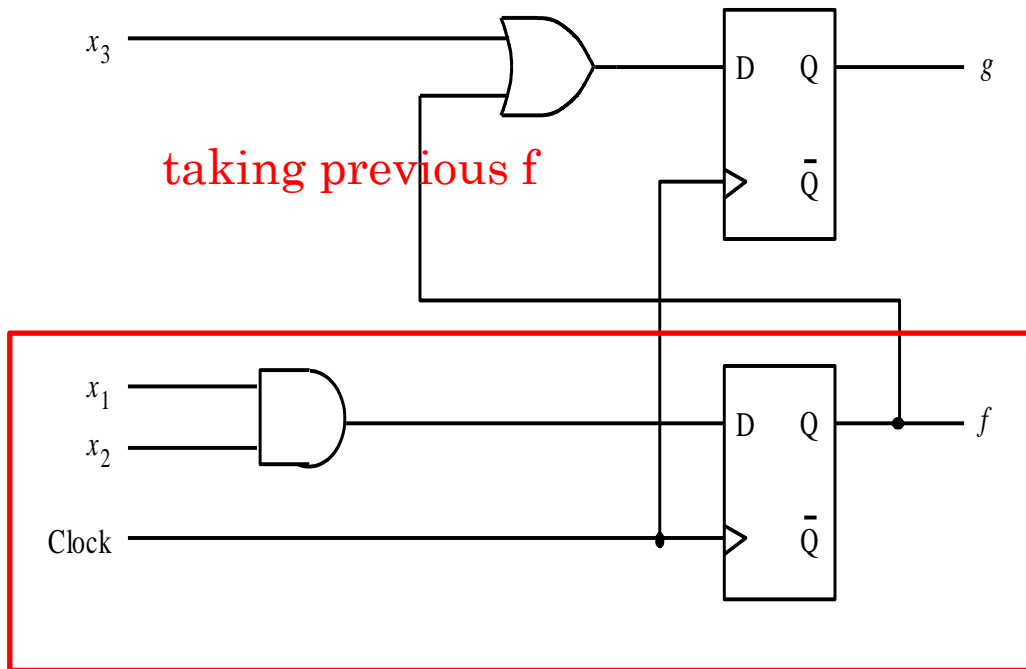

```
module simple (x1, x2, x3,
Clock, f, g);
  input x1, x2, x3, Clock;
  output reg f, g;
```

```
  always @(posedge
Clock)
```

```
  begin
```

```
    f <= x1 & x2;
```

```
    g <= f | x3;
```

```
  end
```

```
endmodule
```

// reversing f and g  
statement makes no  
difference in result.


// Non-blocking assignment, f and g are updated at the same time.  
Meaning that, g must take a previous f.



# PIPELINES USING REGISTERS

Total delay =  $\text{Delay}_1 + \text{Delay}_2 + \text{Delay}_3$

Interval between outputs > Total delay

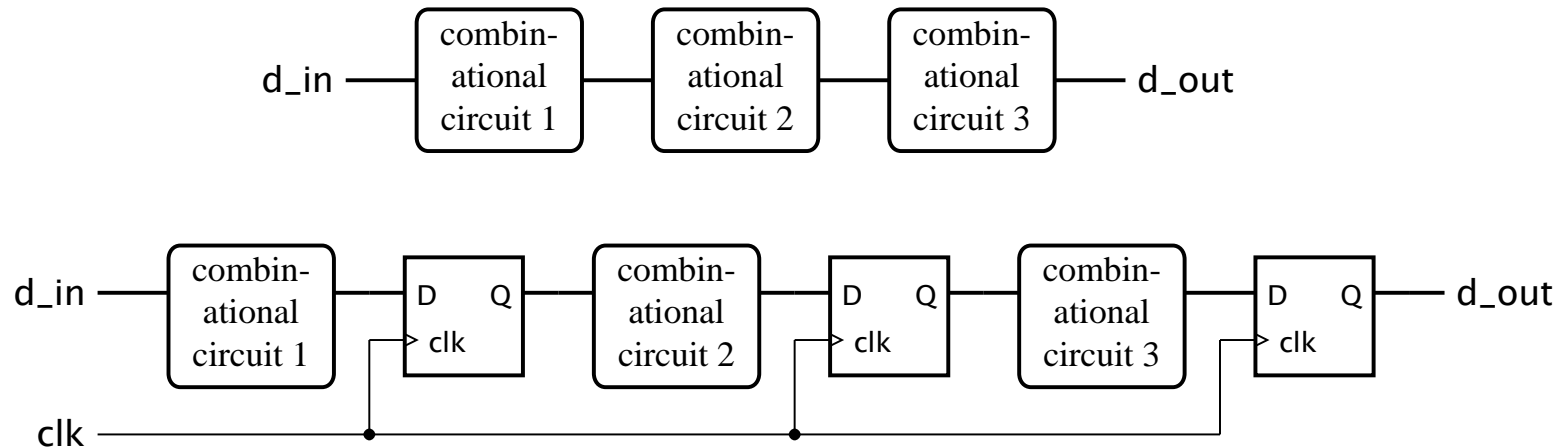

Clock period =  $\max(\text{Delay}_1, \text{Delay}_2, \text{Delay}_3)$

Total delay =  $3 \times \text{clock period}$

Interval between outputs = 1 clock period

## PIPELINE EXAMPLE

DEVELOP A VERILOG MODEL FOR A PIPELINED CIRCUIT THAT COMPUTES THE AVERAGE OF CORRESPONDING VALUES IN THREE STREAMS OF INPUT VALUES, A, B AND C. THE PIPELINE CONSISTS OF THREE STAGES: THE FIRST STAGE SUMS VALUES OF A AND B AND SAVES THE VALUE OF C; THE SECOND STAGE ADDS ON THE SAVED VALUE OF C; AND THE THIRD STAGE DIVIDES BY THREE. THE INPUTS AND OUTPUT ARE ALL SIGNED FIXED-POINT NUMBERS INDEXED FROM 5 DOWN TO -8.

- Compute the average of corresponding numbers in three input streams
  - New values arrive on each clock edge

```
module average_pipeline ( output reg signed [5:-8] avg,  
                        input      signed [5:-8] a, b, c,  
                        input                               clk );  
  
    wire signed [5:-8] a_plus_b, sum, sum_div_3;  
    reg  signed [5:-8] saved_a_plus_b, saved_c, saved_sum;  
    ...
```




# PIPELINE EXAMPLE

```
...  
assign a_plus_b = a + b;  
always @(posedge clk) begin // Pipeline register 1  
    saved_a_plus_b <= a_plus_b;  
    saved_c        <= c;  
end  
assign sum = saved_a_plus_b + saved_c;  
always @(posedge clk) // Pipeline register 2  
    saved_sum <= sum;  
assign sum_div_3 = saved_sum * 14'b000000001010101;  
always @(posedge clk) // Pipeline register 3  
    avg <= sum_div_3;  
endmodule
```
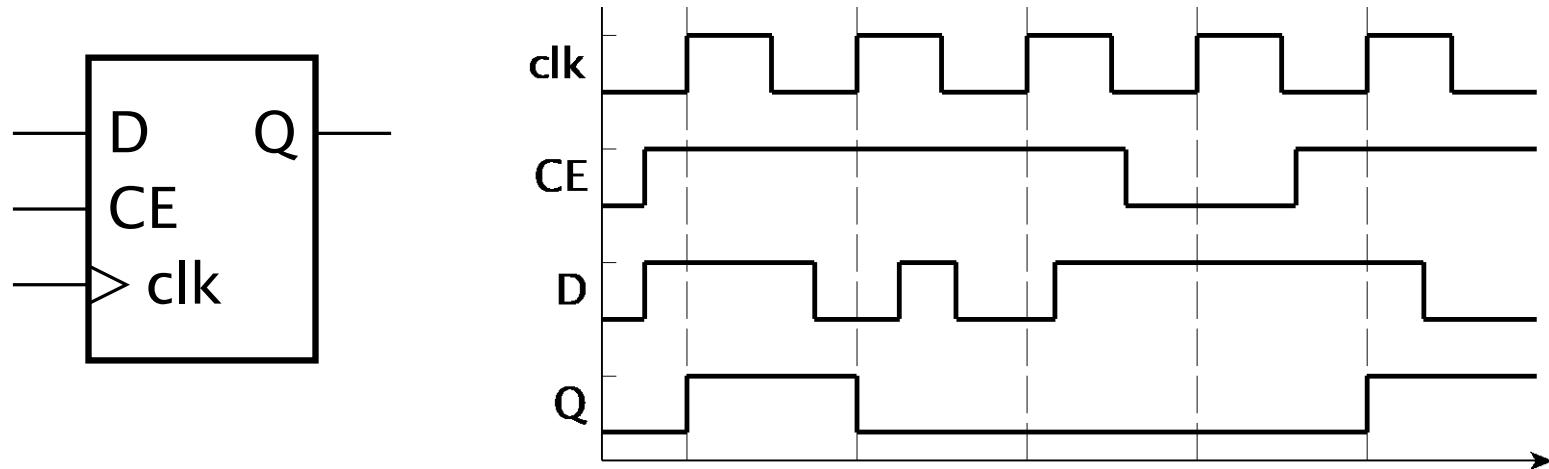
# D-FLIPFLOP WITH ENABLE

- Storage controlled by a clock-enable
  - stores only when  $CE = 1$  on a rising edge of the clock



- CE is a *synchronous control* input


# REGISTER WITH ENABLE

- One flipflop per bit
  - clk and CE wired in common

```
wire [n:0] d;  
wire      ce;  
reg  [n:0] q;  
...  
  
always @(posedge clk)  
    if (ce) q <= d;
```
 
# REGISTER WITH SYNCHRONOUS RESET



- Reset input forces stored value to 0
  - reset input must be stable around rising edge of clk



```
always @(posedge clk)
  if      (reset) q <= 0;
  else if (ce)    q <= d;
```
  
# REGISTER WITH ASYNCHRONOUS RESET

- Reset input forces stored value to 0
  - reset can become 1 at any time, and effect is immediate
  - reset should return to 0 synchronously



# ASYNCH RESET IN VERILOG

```
always @(posedge clk or posedge reset)
  if      (reset) q <= 0;
  else if (ce)    q <= d;
```


- reset is an *asynchronous control* input here
  - include it in the event list so that the process responds to changes immediately

Develop a Verilog model for an accumulator that calculates the sum of a sequence of fixed-point numbers. Each input number is signed with 4 pre-binary-point and 12 post-binary-point bits. The accumulated sum has 8 pre-binary-point and 12 post-binary-point bits. A new number arrives at the input during a clock cycle when the data\_en control input is 1. The accumulated sum is cleared to 0 when the reset control input is 1. Both control inputs are synchronous.

- Sum a sequence of signed numbers
  - A new number arrives when data\_en = 1
  - Clear sum to 0 on synch reset

```
module accumulator
( output reg signed [7:-12] data_out,
  input      signed [3:-12] data_in,
  input      data_en, clk, reset );
wire signed [7:-12] new_sum;
assign new_sum = data_out + data_in;
always @(posedge clk)
  if      (reset)    data_out <= 20'b0;
  else if (data_en) data_out <= new_sum;
endmodule
```

 The symbol in Figure shows a negative-edge-triggered flip-flop with clock enable, negative-logic asynchronous preset and clear, and both active-high and active-low outputs. It is illegal for both preset and clear to be active together. Develop a Verilog model for this flip-flop.



```

module flip_flop_n ( output reg Q,
                    output      Q_n,
                    input       pre_n, clr_n, D,
                    input       clk_n, CE );

    always @( negedge clk_n or
              negedge pre_n or negedge clr_n ) begin
        if ( !pre_n && !clr_n)
            $display("Illegal inputs: pre_n and clr_n both
0");
        if      (!pre_n) Q <= 1'b1;
        else if (!clr_n) Q <= 1'b0;
        else if (CE)    Q <= D;
    end



    assign Q_n = ~Q;
endmodule

```



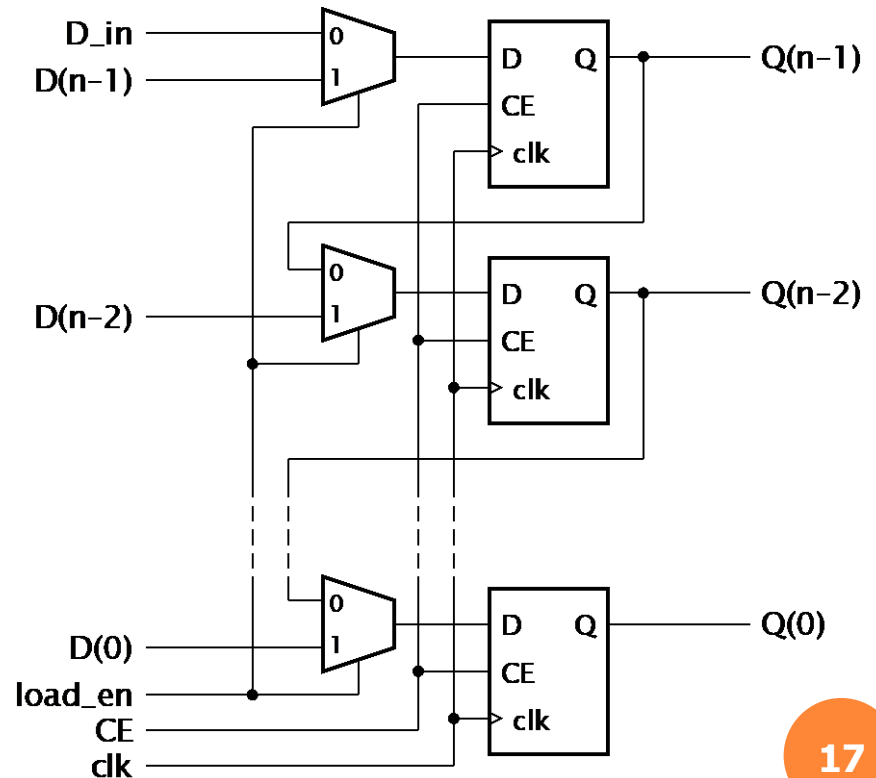 
# SHIFT REGISTERS

- Performs shift operation on stored data
  - Arithmetic scaling
  - Serial transfer of data





we showed how to perform multiplication of unsigned integers by addition of partial products. Construct a multiplier for two 16-bit operands containing just one adder that adds successive partial products over successive clock cycles. The final product is 32 bits.

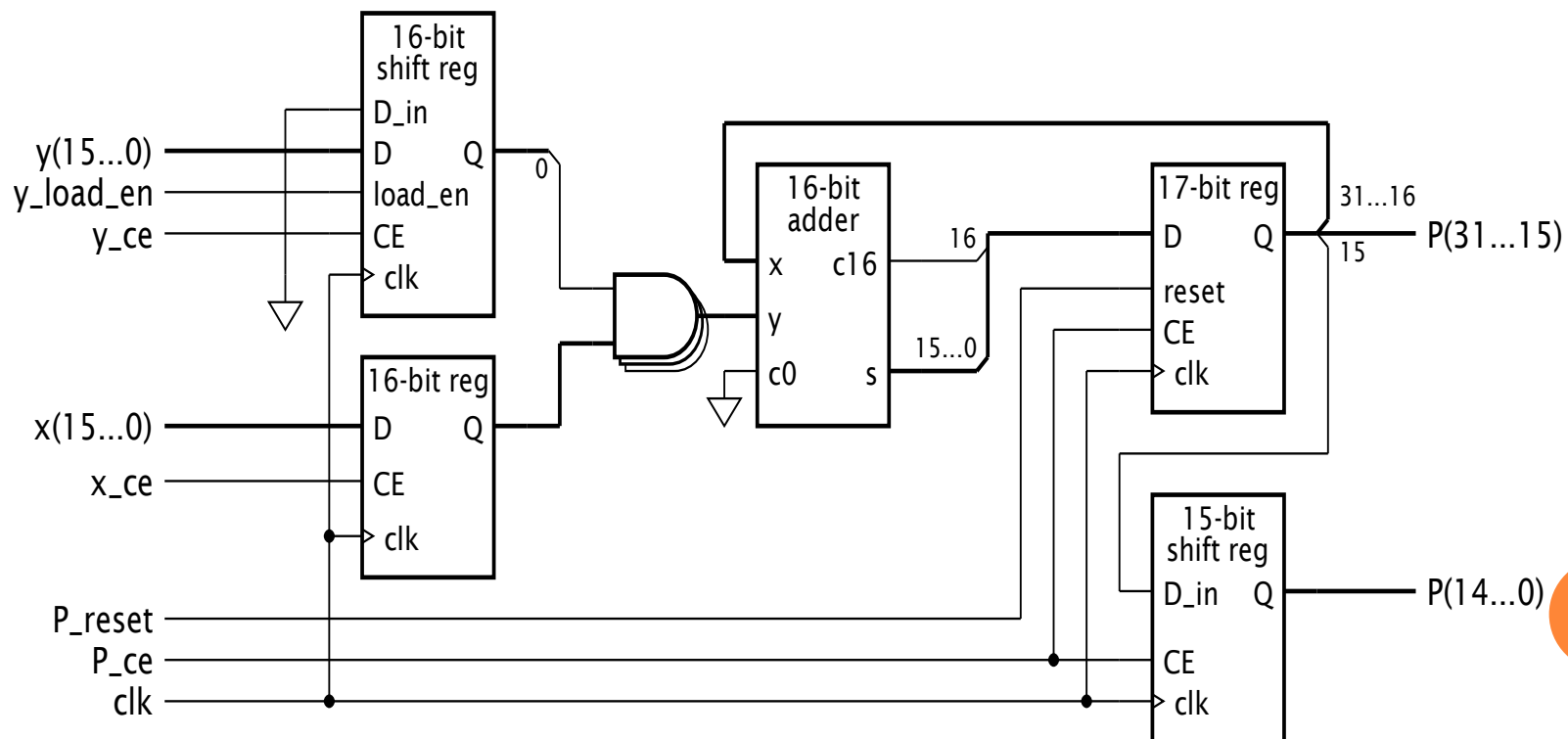- 16×16 multiply over 16 clock cycles, using one adder
  - Shift register for multiplier bits
  - Shift register for LCB's of accumulated product


  
# LATCHES

- Level-sensitive storage
  - Data transmitted while enable is '1'
    - *transparent* latch
  - Data stored while enable is '0'




```
always @(LE or D)
  if(LE) Q <= D;
```

# COUNTERS

- Stores an unsigned integer value
  - increments or decrements the value
- Used to count occurrences of
  - events
  - repetitions of a processing step
- Used as timers
  - count elapsed time intervals by incrementing periodically


# FREE-RUNNING COUNTER

 

- Increments every rising edge of clk
  - up to  $2^n - 1$ , then wraps back to 0
  - i.e., counts modulo  $2^n$
- This counter is *synchronous*
  - all outputs governed by clock edge

 **EXAMPLE 4.6** Design a circuit that counts 16 clock cycles and produces a control signal, ctrl, that is 1 during every eighth and twelfth cycle.

- Count modulo 16 clock cycles
  - Control output = 1 every 8<sup>th</sup> and 12<sup>th</sup> cycle
  - decode count values 0111 and 1011




## DEVELOP A VERILOG MODEL OF THE CIRCUIT SHOWN ABOVE

```
module decoded_counter ( output ctrl,
                        input  clk );

    reg [3:0] count_value;
    always @(posedge clk)
        count_value <= count_value + 1;
    assign ctrl = count_value == 4'b0111 ||
                  count_value == 4'b1011;
endmodule
```

## COUNT ENABLE AND RESET

- Use a register with control inputs

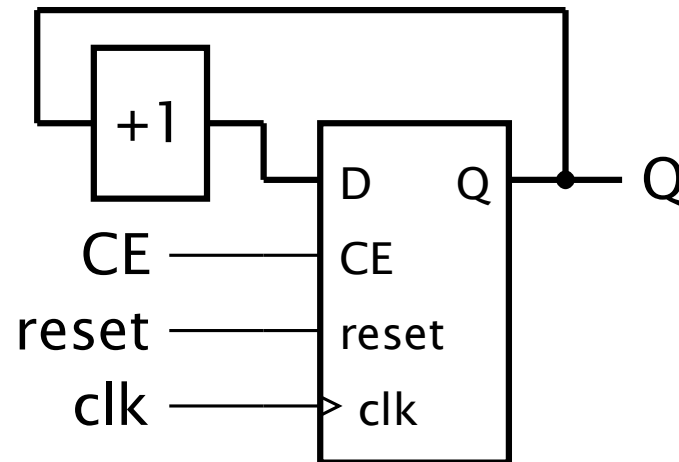


- Increments when  $CE = 1$  on rising clock edge
- Reset: synch or asynch


 
# TERMINAL COUNT


- Status signal indicating final count value



- TC is 1 for one cycle in every  $2^n$  cycles
  - frequency = clock frequency /  $2^n$
- Called a *clock divider*

A digital alarm clock needs to generate a periodic signal at a frequency of approximately 500Hz to drive the speaker for the alarm tone. Use a counter to divide the system's master clock signal, with a frequency of 1 MHz, to derive the alarm tone.

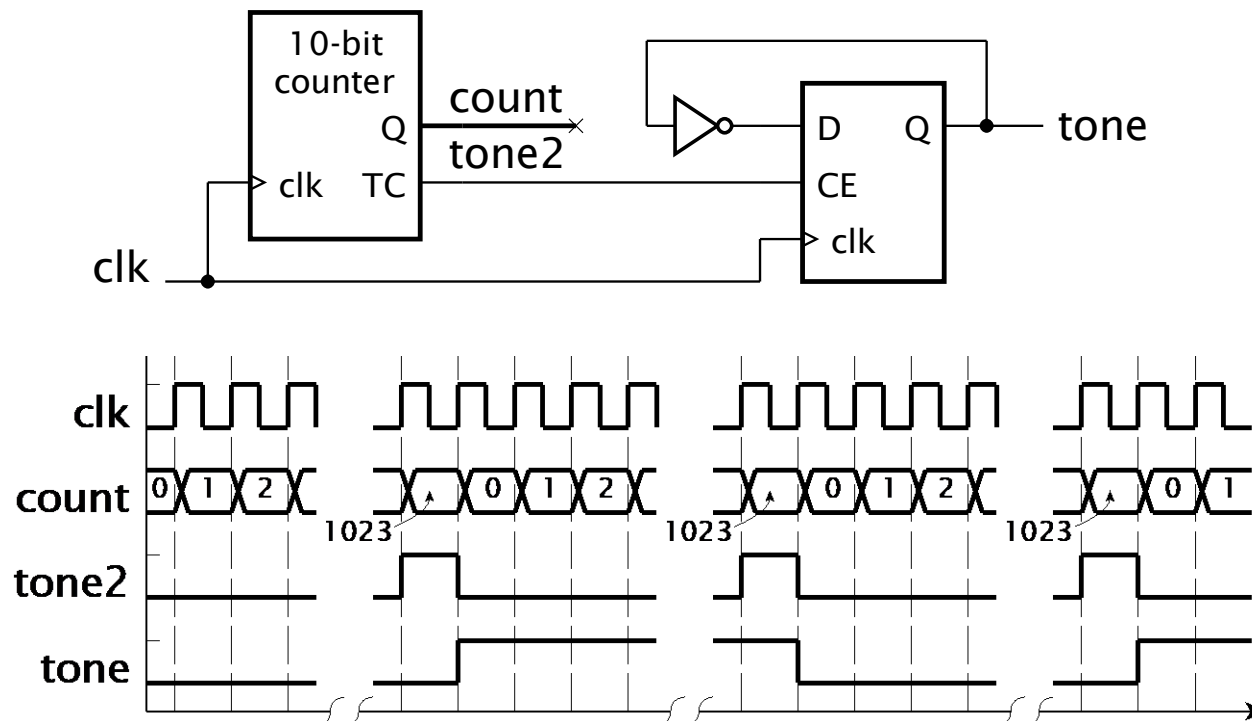
We need to divide the master clock signal by approximately 2000. We can use a divisor of  $2^{11} = 2048$ , which gives us an alarm tone frequency of 488Hz, which is close enough to 500 Hz. Thus, we could use the terminal-count output of an 11-bit counter for the tone signal.



Divide by  $k$ :

Design a circuit for a modulo 10 counter, otherwise known as a *decade counter*.

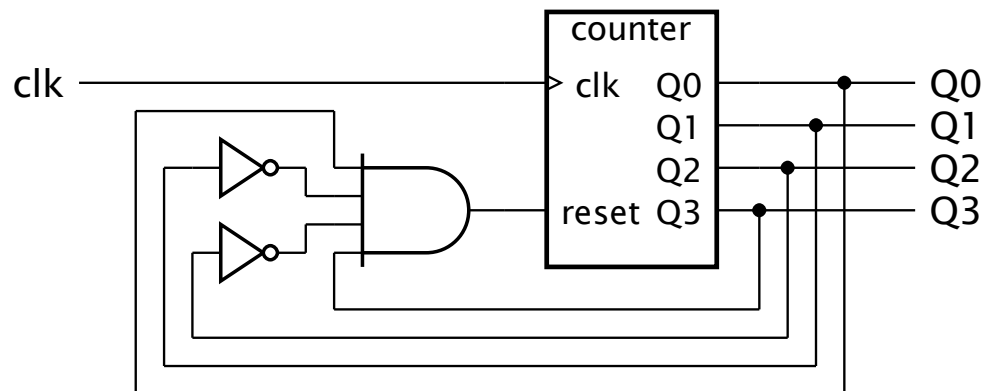- Decode  $k-1$  as terminal count and reset counter register
  - Counter increments modulo  $k$
- Example: decade counter
  - Terminal count = 9




# DECADE COUNTER IN VERILOG

Develop a Verilog model for the decade counter shown in above example

```
module decade_counter ( output reg [3:0] q,  
                        input          clk );  
    always @(posedge clk)  
        q <= q == 9 ? 0 : q + 1;  
endmodule
```
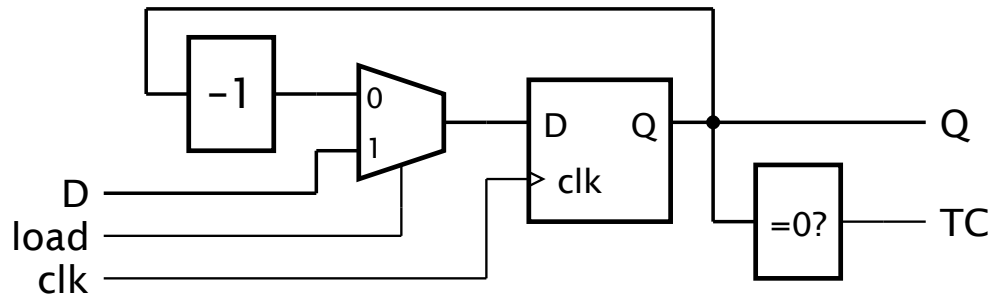
# DOWN COUNTER WITH LOAD

- Load a starting value, then decrement
  - Terminal count = 0
- Useful for interval timer



## LOADABLE COUNTER IN VERILOG

Develop a Verilog model for an interval timer that has clock, load and data input ports and a terminal-count output port. The timer must be able to count intervals of up to 1000 clock cycles.

```
module interval_timer_rtl ( output      tc,
                           input [9:0] data,
                           input      load, clk );

    reg [9:0] count_value;
    always @(posedge clk)
        if (load) count_value <= data;
        else      count_value <= count_value - 1;
    assign tc = count_value == 0;
endmodule
```

# RELOADING COUNTER IN VERILOG

Modify the interval timer so that, when it reaches zero, it reloads the previously loaded value rather than wrapping around to the largest count value.


```
module interval_timer_repetitive ( output      tc,
                                   input [9:0] data,
                                   input      load, clk );

    reg [9:0] load_value, count_value;


    always @(posedge clk)
        if (load) begin
            load_value <= data;
            count_value <= data;
        end
        else if (count_value == 0)
            count_value <= load_value;
        else
            count_value <= count_value - 1;

    assign tc = count_value == 0;
endmodule
```

# RIPPLE COUNTER

 

 - Each bit toggles between 0 and 1
  - when previous bit changes from 1 to 0





# RIPPLE OR SYNCH COUNTER?

- Ripple counter is ok if
  - length is short
  - clock period long relative to flipflop delay
  - transient wrong values can be tolerated
  - area must be minimal
- E.g., alarm clock
- Otherwise use a synchronous counter

# TEST BENCH:

A testbench is simply a Verilog module.

A design under test, abbreviated as DUT, is a synthesizable module of the functionality we want to test. In other words, it is the circuit design that we would like to test. We can describe our DUT using one of the three modeling styles in Verilog – Gate-level, Dataflow, or Behavioral.

```
module and_gate(c,a,b);  
  
input a,b;  
output c;  
  
assign c = a & b;  
  
endmodule
```



```
module and_tb;
  reg A,B;
  wire C;
  and_gate dut(.a(A), .b(B), .c(C));
  initial
  begin
    #5 A =0; B=0;
    #5 A =0; B=1;
    #5 A =1; B=0;
    #5 A =1; B=1;
  end
  initial
  begin
    $monitor("simtime = %g, A =%b, B =%b, C =%b", $time,A,B,C);
  end
endmodule
```

## Steps:

- Start with the module declaration
- Declare reg and wire

The reg data type will hold the value until a new value is assigned to it. This is used to apply a stimulus to the inputs of DUT

The wire data type is similar to that of a physical connection. It will hold the value that is driven by a port, assign statement, or reg. This is used to check the output signals *from* the DUT.

- DUT Instantiation

```
<dut_module><instance_name>(<dut_signal>(test_modu  
le_signal),.....)
```

Instance\_name is user defined name



## ○ Initial and Always blocks

There are two sequential blocks in Verilog, initial and always. It is in these blocks that we apply the stimulus.

The following is the stimulus for and\_gate in the initial block

```
initial
begin
A = 0; B = 0; // starts execution at t=0
#10 A = 0; B = 1; // execution at t = 10 time units
#10 A = 1; B = 0; // execution at t = 20 time units
#10 A = 1; B = 1; //execution at t = 30 time units
end
```



an always block repeatedly executes, although the execution starts at time  $t=0$ .

The following is the stimulus for and\_gate in the always block

```
module always_block_example;  
  reg clk;  
  
  initial  
  begin  
    clk = 0;  
  end  
  
  always  
    #10 clk = ~clk;  
endmodule
```



## ○ Simulation

- During simulation, the designer should know the status of the current simulation. Hence, a printout of the simulation result is essential, which will inform the designer. The value of all the signals should be displayed as it helps for debugging purposes. Therefore, while writing testbench, we can use two system tasks to print the simulation results.

### **\$display**

This is an important system task available in Verilog. It is used for displaying values of variables or strings or expressions. This inserts a newline by default at the end of the string. Let's see how we can use a \$display to print signals in a test bench:

```
$display( "time = %g, A = %b, B = %b, C =%b", $time, A,B,C);
```

- The characters mentioned in the quotes will be printed as it is. The letter along with % denotes the string format. We use %b to represent binary data. We can use %d, %h, %o for representing decimal, hexadecimal, and octal, respectively. The %g is used for expressing real numbers.
- As the name states, it is clear that it will monitor the data or variable for which it is written, and whenever the variable changes, it will print the changed value.





- <https://technobyte.org/testbench-in-verilog/>

