



**DEPARTMENT  
OF  
ELECTRONICS & COMMUNICATION ENGINEERING HDL LABORATORY MANUAL  
V Semester (19EC5DLHDL)  
Autonomous Course 2021**



**HOD : Dr. Manjunath T C  
In -Charge: Dr. Rajagopal A.**

<b>Name of the Student</b>	:	
<b>Semester /Section</b>	:	
<b>USN</b>	:	
<b>Batch</b>	:	

**Dayananda Sagar College of Engineering Shavige Malleshwara Hills, Kumaraswamy  
Layout,**

**Banashankari, Bangalore-560078, Karnataka**

**Tel : +91 80 26662226 26661104 Extn : 2731 Fax : +90 80 2666 0789 Web -  
<http://www.dayanandasagar.edu> Email : [hod-ece@dayanandasagar.edu](mailto:hod-ece@dayanandasagar.edu) ( An Autonomous  
Institute Affiliated to VTU, Approved by AICTE & ISO 9001:2008 Certified ) ( Accredited  
by NBA, National Assessment & Accreditation Council (NAAC) with 'A' grade )**

## HDL LAB

1. Write HDL code to realize all the logic gates.
2. Write a HDL code to describe the functions of a Full Adder using three modelling styles and full adder using Half adder.
3. Write HDL code for 4-bit ripple carry adder using full adders.
4. Write HDL code for Adder/Subtractor circuit
5. Write a HDL program for the following combinational designs
  - a. 2 to 4 Decoder.
  - b. 8 to 3 Encoder (without priority & with priority).
  - c. 8 to 1 Multiplexer.
  - d. De-multiplexer
  - e. 4 bit Binary to Gray converter.
  - f. 4 bit Gray to Binary converter
  - g. Comparator
6. Write HDL code for BCD Adder
7. Develop the HDL code for the following flip-flops
  - a. D Flip-Flop
  - b. JK Flip-Flop
  - c. T Flip-Flop
8. Write a model for 8bit ALU. ALU should use combinational logic to calculate an output based on the 3-bit op-code input. ALU should decode the 3-bit op-code according to the given in example below. Opcode (2:0)

OPCODE	ALU OPERATION
1.	A + B
2.	A – B
3.	A Complement
4.	A * B
5.	A AND B
6.	A OR B
7.	A NAND B
8.	A XOR B
9. Design 4 bit Binary counters (Synchronous reset and Asynchronous reset) and any sequence Counters.
10. Design 4 bit BCD counters(Synchronous reset and Asynchronous reset)
11. Design Mealy and Moore state machine for a given sequence.
12. Stepper motor
13. VGA Display
14. RAM

TOOLS used: Modelsim/Quartus Prime Standard edition 20.1/De-Sim/Iverilog/Xilinx ISE.

Experiment No: 1

Date: \_\_\_\_\_

## LOGIC GATES

**Aim:** Write a HDL code to realize all LOGIC GATES.

### Verilog

```
module logicgates(a,b,y);  
input a,b;  
output[6:0] y;  
assign y[0] = ~a;  
assign y[1] = a & b;  
assign y[2] = a|b;  
assign y[3] = ~(a&b);  
assign y[4] = ~(a|b);  
assign y[5] = a^b;  
assign y[6] = ~(a^b);  
endmodule
```

### Test Bench

### Results

Experiment No: 2

Date: \_\_\_\_\_

## **FULL ADDER**

**Aim:** Write a HDL code FULL ADDER in all styles.

1. DATA FLOW
2. BEHAVIORAL
3. STRUCTURAL

### **1. DATA FLOW**

#### **Verilog**

```
module fulladder_df (a, b, cin, sum, cout);  
input a, b, cin;  
output sum, cout;  
assign sum = a^b^cin;  
assign cout = (a&b)|(b&cin)|(a&cin);  
endmodule
```

### **2. BEHAVIORAL**

#### **Verilog**

```
module fulladder_bh( a, b, cin, sum, cout);  
input a, b, cin;  
output sum,cout;  
reg sum,cout;  
always @(a,b,cin)  
{cout,sum}=a+b+cin;  
endmodule
```

### **3. STRUCTURAL**

#### **Verilog**


```
module fulladder_str (a, b, cin, sum, cout); input a, b, cin;  
output sum, cout; wire s1,s2,s3;  
xor x1(sum,a,b,cin);
```

```

and a1(s1,a,b);
and a2(s2,a,cin);
and a3(s3,b,cin);
or o1(cout,s1,s2,s3);
endmodule

```

**Aim:** Full adder using Halfadder

 

```

module half_adder(S, C, A, B);
output S, C;
input A, B;
assign S = A ^ B;
assign C = A & B;
endmodule

module full_adder(sum, cout, in1, in2, cin);
output sum, cout;
input in1, in2, cin;
wire I1, I2, I3;
half_adder ha1(I1, I2, in1, in2);
half_adder ha2(sum, I3, I1, cin);
assign cout = I2 || I3;
endmodule

```

**Test Bench**

**Results**

Experiment No: 3

Date: \_\_\_\_\_

## **RIPPLE CARRY ADDER**

**Aim:** Write a HDL code for Ripple Carry Adder

### **Verilog**

```
module fulladder(a, b, cin, sum, cout);  
input a, b, cin;  
output sum, cout;  
assign sum = a^b^cin;  
assign cout = (a&b)|(b&cin)|(a&cin);  
endmodule
```

```
module ripple_add(a,b,cin,s,carry,);  
output [3:0]s;  
output carry;  
input [3:0]a,b;  
input cin;  
wire c1,c2,c3;  
fulladder f1(a[0],b[0],cin,s[0],c1);  
fulladder f2(a[1],b[1],c1,s[1],c2);  
fulladder f3(a[2],b[2],c2,s[2],c3);  
fulladder f4(a[3],b[3],c3,s[3],carry);  
endmodule
```

**Test Bench:**

**Results**

**ADDER SUBTRACTOR**

**Aim:** Write a HDL code for Ripple Carry Adder Subtractor

**Verilog**

```
module adder_subtractor(S, C, V, A, B, Op);  
    output [3:0] S; // The 4-bit sum/difference.  
    output      C; // The 1-bit carry/borrow status.  
    output      V; // The 1-bit overflow status.  
    input [3:0] A; // The 4-bit augend/minuend.  
    input [3:0] B; // The 4-bit addend/subtrahend.  
    input      Op; // The operation: 0 ==> Add, 1 ==> Subtract.  
  
    wire C0; // The carry out bit of fa0, the carry in bit of fa1.  
    wire C1; // The carry out bit of fa1, the carry in bit of fa2.  
    wire C2; // The carry out bit of fa2, the carry in bit of fa3.  
    wire C3; // The carry out bit of fa2, used to generate final carry/borrow.  
  
    wire B0; // The xor'd result of B[0] and Op  
    wire B1; // The xor'd result of B[1] and Op  
    wire B2; // The xor'd result of B[2] and Op  
    wire B3; // The xor'd result of B[3] and Op  
    // Looking at the truth table for xor we see that  
    // B xor 0 = B, and  
    // B xor 1 = not(B).  
    // So, if Op==1 means we are subtracting, then  
    // adding A and B xor Op along with setting the first  
    // carry bit to Op, will give us a result of  
    // A+B when Op==0, and A+not(B)+1 when Op==1.
```

```

// Note that not(B)+1 is the 2's complement of B, so
// this gives us subtraction.
xor(B0, B[0], Op);
xor(B1, B[1], Op);
xor(B2, B[2], Op);
xor(B3, B[3], Op);
xor(C, C3, Op);    // Carry = C3 for addition, Carry = not(C3) for subtraction.
xor(V, C3, C2);    // If the two most significant carry output bits differ, then we have an
overflow.

```

```

full_adder fa0(S[0], C0, A[0], B0, Op); // Least significant bit.
full_adder fa1(S[1], C1, A[1], B1, C0);
full_adder fa2(S[2], C2, A[2], B2, C1);
full_adder fa3(S[3], C3, A[3], B3, C2); // Most significant bit.
endmodule // ripple_carry_adder_subtractor

```

```

module full_adder (sum, cout,a, b, cin, );
input a, b, cin;
output sum, cout; wire s1,s2,s3;
xor x1(sum,a,b,cin);
and a1(s1,a,b);
and a2(s2,a,cin);
and a3(s3,b,cin);
or o1(cout,s1,s2,s3);
endmodule

```

**Test Bench:**

**Results**



Experiment No:5a

Date: \_\_\_\_\_

## **DECODER (2:4)**

**Aim:** Write a HDL code to design 2:4 DECODER

### **Verilog**

```
module decoder(I,D);  
input [1:0] I;  
output [3:0] D;  
reg [3:0] D;  
always @(I)  
begin  
if (I==2'B00) D=4'B0001;  
else if (I==2'B01) D=4'B0010;  
else if (I==2'B10) D=4'B0100;  
else if (I==2'B11) D=4'B1000;  
else D=4'BZZZZ;  
end  
endmodule
```

### **Test Bench**

### **Results**

Experiment No:5b

Date: \_\_\_\_\_

## **ENCODER (8:3)**

**Aim:** Write a HDL code to design 8:3 ENCODER with and without priority.

### **Without priority Verilog**

```
module encoder_wop (I,D);  
input [7:0] I;  
output [2:0] D;  
reg [2:0] D;  
always @(I)  
begin  
case (I)  
8'd1 : D=3'd0;  
8'd2 : D=3'd1;  
8'd4 : D=3'd2;  
8'd8 : D=3'd3;  
8'd16 : D=3'd4;  
8'd32 : D=3'd5;  
8'd64 : D=3'd6;  
8'd128 : D=3'd7;  
default: D=3'BZZZ;  
endcase  
end  
endmodule
```

### **Test Bench**

### **With Priority Verilog**

```
module encoder_wp (I,D);  
input [7:0] I;  
output [2:0] D;  
reg [2:0] D;  
always @(I)  
begin  
if (I[7]==1'B1) D=3'B111;  
else if (I[6]==1'B1) D=3'B110;  
else if (I[5]==1'B1) D=3'B101;  
else if (I[4]==1'B1) D=3'B100;  
else if (I[3]==1'B1) D=3'B011;  
else if (I[2]==1'B1) D=3'B010;  
else if (I[1]==1'B1) D=3'B001;  
else if (I[0]==1'B1) D=3'B000;  
else D=3'BZZZ;  
end  
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 5c

Date: \_\_\_\_\_

## **MULTIPLEXER (8:1)**

**Aim:** Write a HDL code to design 8:1 MULTIPLEXER

### **Verilog**

```
module mux8_1 (I, S, D);  
input [7:0] I;  
input [2:0] S;  
output D;  
reg D;  
always @ (I, S)  
begin  
    case(S)  
        3'd0: D=I[0];  
        3'd1: D=I[1];  
        3'd2: D=I[2];  
        3'd3: D=I[3];  
        3'd4: D=I[4];  
        3'd5: D=I[5];  
        3'd6: D=I[6];  
        3'd7: D=I[7];  
        default: D=1'BZ;  
    endcase  
end  
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 5d

Date: \_\_\_\_\_

## **DEMULTIPLEXER**

**Aim:** Write a HDL code to design 1:8 DEMULTEPLEXER

### **Verilog**

```
module demux1_8(I,S,D);  
input I;  
input [2:0] S;  
output [7:0]D;  
reg [7:0]D;  
always @(I,S)  
begin  
D=8'd0;  
CASE (S)  
3'd0 : D[0]=I;  
3'd1 : D[1]=I;  
3'd2 : D[2]=I;  
3'd3 : D[3]=I;  
3'd4 : D[4]=I;  
3'd5 : D[5]=I;  
3'd6 : D[6]=I;  
3'd7 : D[7]=I;  
default: D=8'B00000000;  
endcase  
end  
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 5e

Date: \_\_\_\_\_

## **BINARY TO GRAY**

**Aim:** Write a HDL code to convert 4-bit BINARY TO GRAY

### **Verilog**

```
module bin_to_gray(B,G);  
input [3:0] B;  
output [3:0] G;  
assign G[3] = B[3];  
assign G[2] = B[3]^B[2];  
assign G[1] = B[2]^B[1];  
assign G[0] = B[1]^B[0];  
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 5f

Date: \_\_\_\_\_

## **GRAY TO BINARY**

```
module gray_to_bin  
    (input [3:0] G, //gray code output  
     output [3:0] bin //binary input );  
    assign bin[3] = G[3];  
    assign bin[2] = G[3] ^ G[2];  
    assign bin[1] = G[3] ^ G[2] ^ G[1];  
    assign bin[0] = G[3] ^ G[2] ^ G[1] ^ G[0];  
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 5g

Date: \_\_\_\_\_

## COMPARATOR

**Aim:** Write a HDL code to design 4-bit comparator.

### Verilog

```
module comparator (a, b, alb, aeb, agb)
input[3:0] a, b;
output alb, aeb, agb;
reg alb, aeb, agb;
always@(a,b)
begin
if(a<b)
begin
alb=1'b1; aeb=1'b0; agb=1'b0;
end
else if (a>b)
begin
alb=1'b0; aeb=1'b0; agb=1'b1;
end
else
begin
alb=1'b0; aeb=1'b1; agb=1'b0;
end
end
endmodule
```

### **Test Bench**

### **Results**

Experiment No: 6

Date: \_\_\_\_\_

## **BCD ADDER**

### **Verilog**

//module declaration with inputs and outputs

```
module bcd_adder(a,b,carry_in,sum,carry);
```

```
    input [3:0] a,b;
```

```
    input carry_in;
```

```
    output [3:0] sum;
```

```
    output carry;
```

```
    //Internal variables
```

```
    reg [4:0] sum_temp;
```

```
    reg [3:0] sum;
```

```
    reg carry;
```

```
    always @(a,b,carry_in)
```

```
    begin
```

```
        sum_temp = a+b+carry_in; //add all the inputs
```

```
        if(sum_temp > 9) begin
```

```
            sum_temp = sum_temp+6; //add 6, if result is more than 9.
```

```
            carry = 1; //set the carry output
```

```
            sum = sum_temp[3:0]; end
```

```
        else
```

```
            begin
```

```
                carry = 0;
```

```
                sum = sum_temp[3:0];
```

```
            end
```

```
        end
```

```
    endmodule
```

### **Test Bench**

### **Results**